

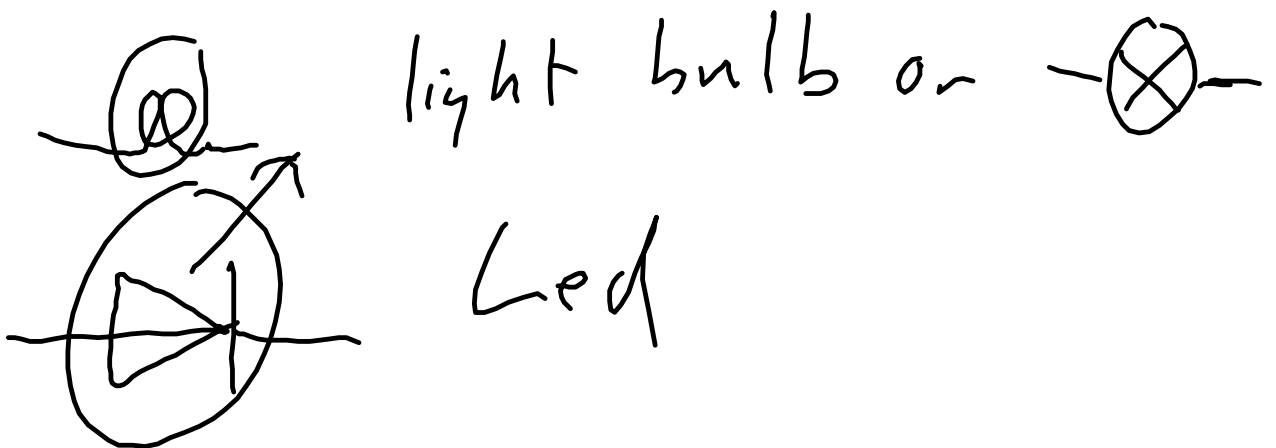


Ohm's "Law" and Power

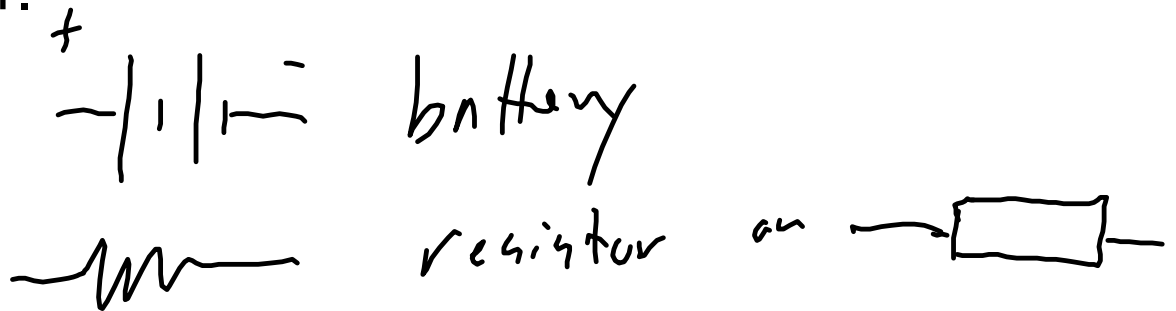Look at a circuit with a 6.0 V battery connected to a 330 ohm resistor and a LED light with an ammeter and a voltmeter connected across the resistor.




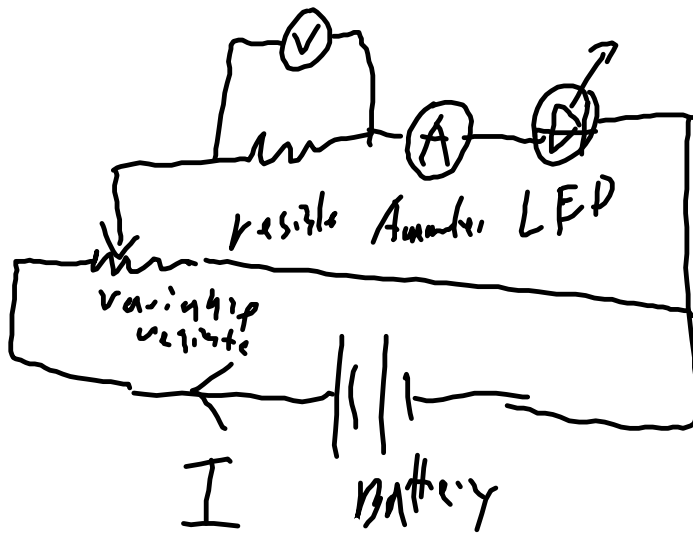

current
- opposite e^- flow

$V(V)$	$I (mA)$
0.0	0.0
0.5	1.6
0.6	2.1
1.0	3.3
2.1	6.6
3.0	9.5
3.5	10.8

Ohmic Resistor

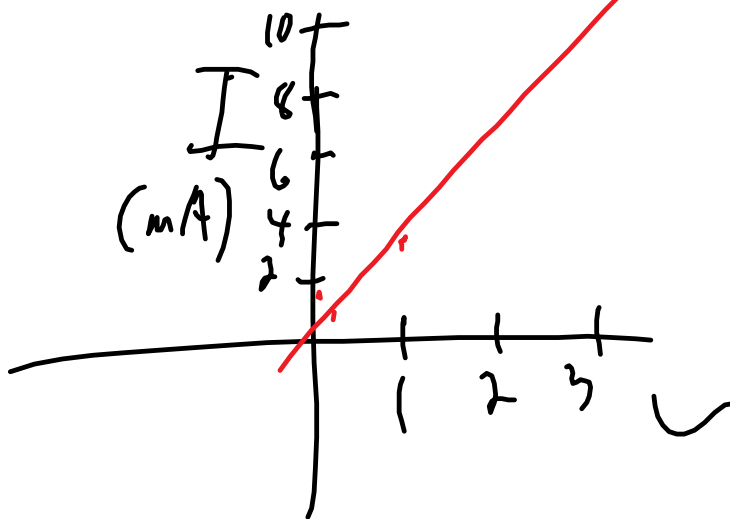

I vs V
constant
slope

$$\text{slope} = \frac{I}{V} = \frac{1}{R}$$

define resistance as
the ratio of $\frac{V}{I} = R$

$$\text{units ohms, } \Omega = \frac{V}{A}$$

Resistors are circuit elements that dissipate electrical energy as heat.

Resistance is the ratio of V/I influences the current for particular applied voltages.

Most resistors are constructed to have a constant resistance over a range of voltages. Ohmic.

Diodes alter their resistance depending on the voltage - not ohmic.

The rate of energy transferred into heat by a resistor or light by a LED is the power output of that circuit element.

$$P = \text{energy/time} \quad V = \text{energy}/\cancel{\text{charge}} \quad I = \cancel{\text{charge}}/\text{time}$$

$P = VI$ for a circuit element
Using ohm's law

$$P = V^2/R = I^2 R = VI$$

For the above circuit, when the voltage across

the resistor is 3.0V the current is 9.5mA.


Determine


- The resistance of the resistor from that data and compare to the listed value of 330 ohms.
- The power output of the resistor.
- How many electrons pass through the resistor per unit time?
- If the voltage across the LED is 1.9V what is its resistance? (current is 9.5mA for both because they are in series)


Ohm's Law and Power



Set up a circuit with a 6.0 V battery connected to a variable resistor, a 330 ohm resistor and a light emitting diode (LED) with voltmeters across the resistor and diode and an ammeter for the current through the resistor and diode.

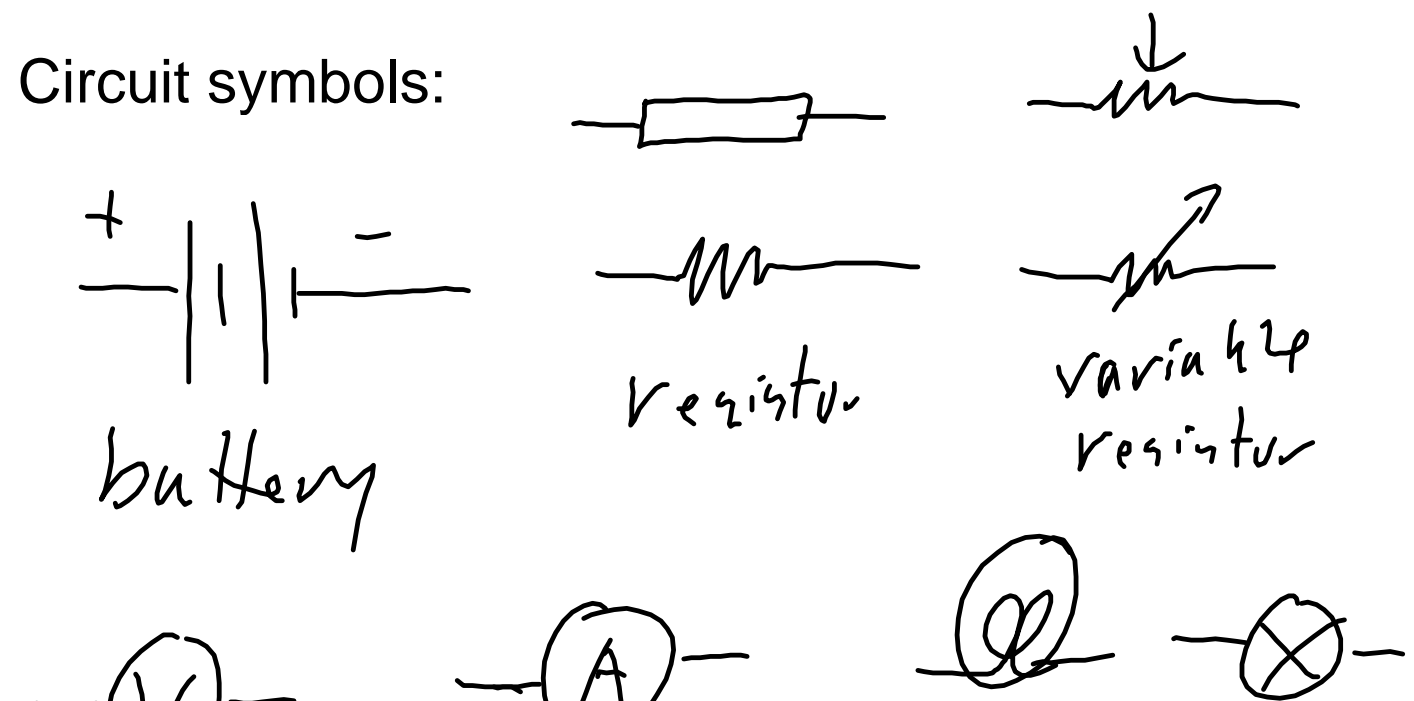
Circuit symbols:

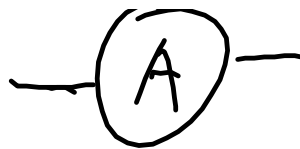



 Voltmeter
 - Parallel



 Ammeter
 - Series

 
 lamp lamp

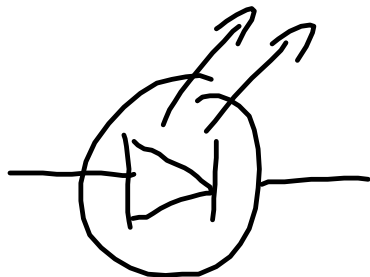
 LED

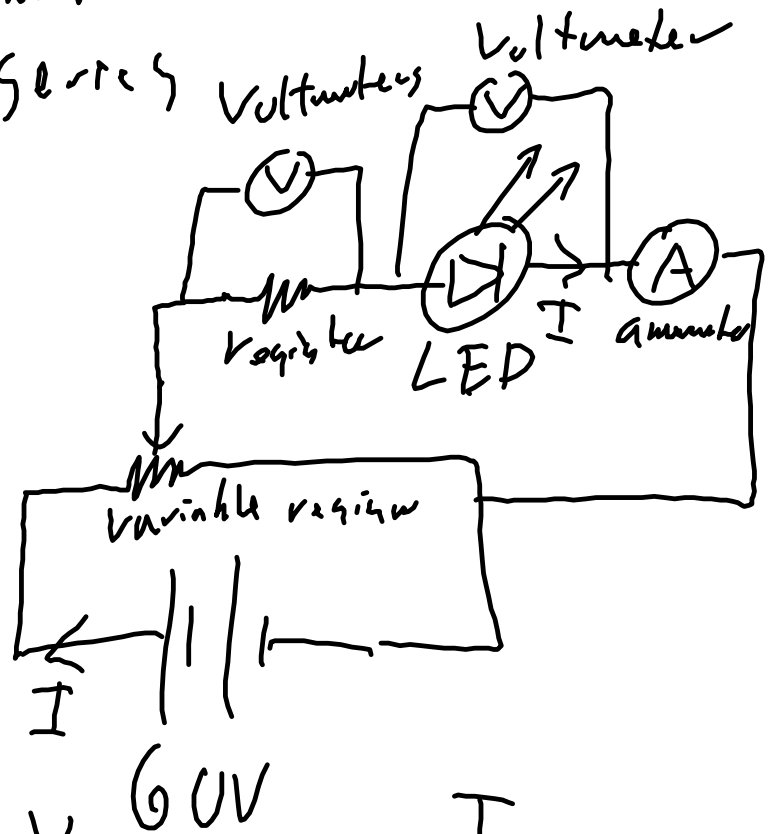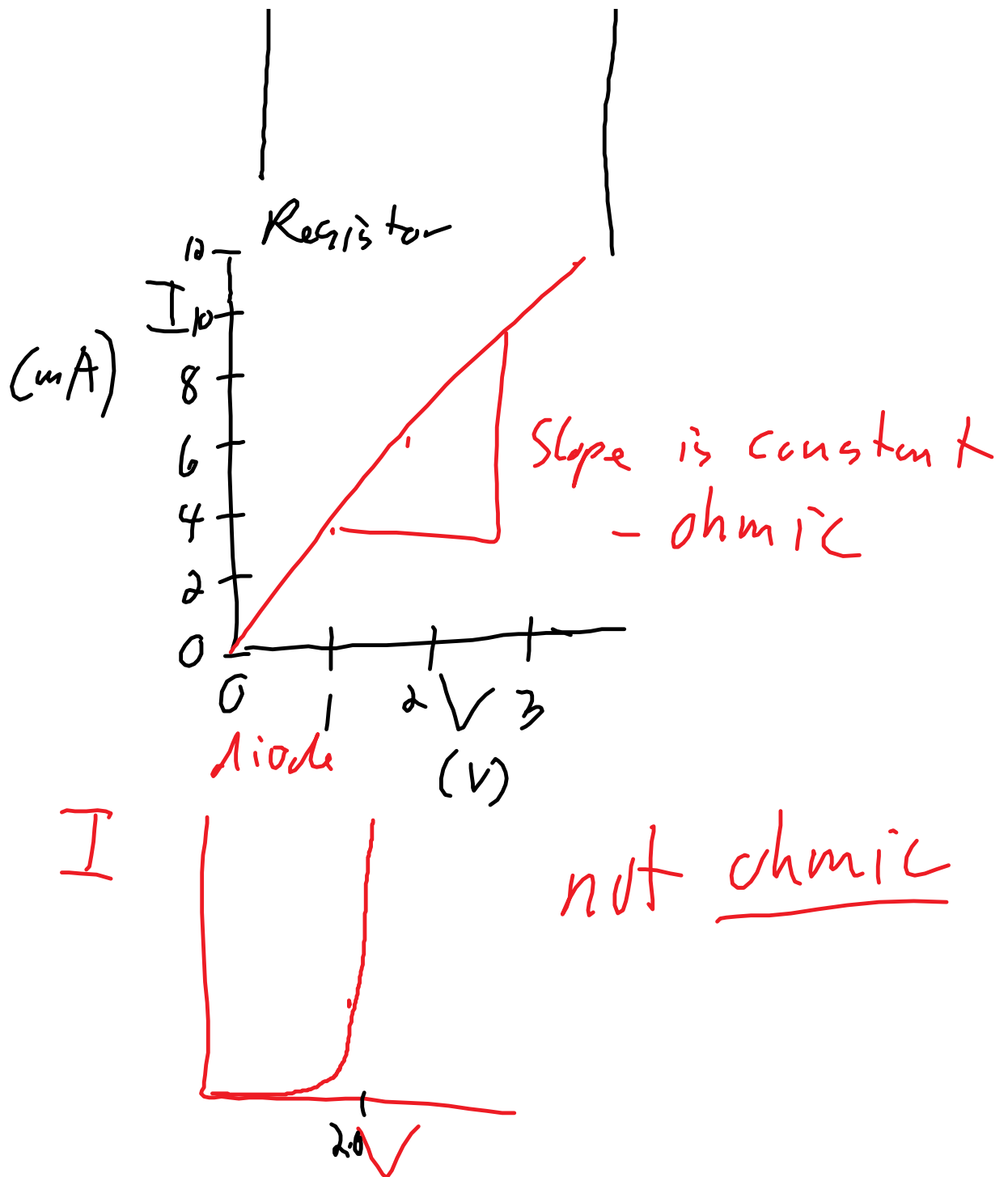

V_1 V of Resistor (V)	V_2 V of diode (V)	I Current (mA)
1.1	1.8	3.5
1.9	1.8	5.8
2.9	1.8	8.9
3.7	1.9	11.0
0.5	0.18	16



Resistor - a circuit element that dissipates electrical energy as heat.

Usually constructed to be ohmic - the resistance is constant over a variety of voltages and currents.

Resistance, R is the ratio of Voltage and current.
 $R = V/I$

Something with high resistance will have low current for a set voltage.

Units: ohm, $\Omega = \text{V/A}$

LED is not ohmic - the resistance changes with different voltages and currents.

Power, P is rate of doing work or the rate of change in energy.

$P = \text{energy/time}$ $V = \text{energy/charge}$ $I = \text{charge/time}$

$$P = W/t = VI = V^2/R = I^2R$$

Eg. In our circuit, when the voltage across the resistor is 3.7V the current was 11.0 mA and the voltage of the diode was 1.9V

- a) What is the resistance of the two devices at that current?
- b) What is the power output of the devices?
- c) When the voltage of the resistor is 1.1V, the current was 3.5mA and diode voltage was 1.8V. What is the resistance and power output of each?

a) $R = V/I = 3.7\text{V} / 11.0\text{mA} = 0.33 \text{ k}\Omega = 330\Omega$ For

the resistor

For the diode $R = 1.9V / 11.0mA = 173\Omega$

b) $P = VI = 3.7V \times 11.0 mA = 3.7 \times 11 = 40.7 = 41 \text{ mW}$
 $P = 1.9 \times 11 = 20.9 = 21 \text{ mW}$


c) $R = V/I = 1.1V / 3.5mA = 1.1/3.5 = 0.3143 = 310\Omega$ For the resistor
For the diode $R = 1.8V / 3.5mA = 1.8/3.5 = 0.5143 = 510\Omega$

$P = VI = 1.1V \times 3.5 \text{ mA} = 1.1 \times 3.5 = 3.85 = 3.8 \text{ mW}$
 $P = 1.8 \times 3.5 = 6.3 \text{ mW}$ for the diode

J lab

$$D = \frac{1}{2} \frac{e \left(\frac{0.06}{2} + L \right) V}{dV_g}$$
$$D = \frac{1}{2} \frac{(0.06) \left(\frac{0.06}{2} + 0.2 \right) 150V}{0.02 (500V)}$$
$$= 0.1035 \text{ m} = \boxed{0.10 \text{ m}}$$


10.4 cm

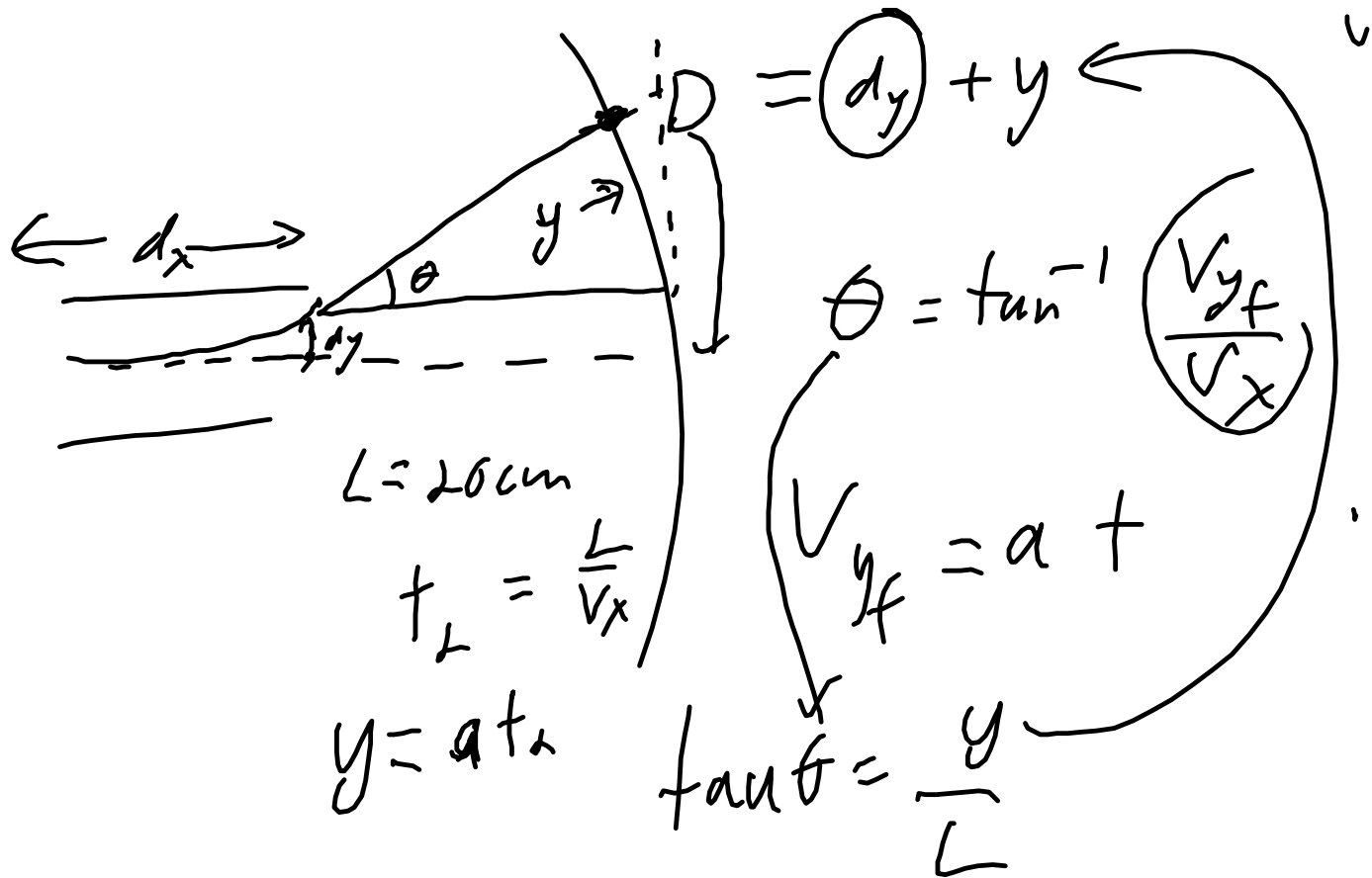





Ohm's "Law" and Power

We have a circuit setup with a battery connected to a variable resistor (also called potentiometer or rheostat) then we have a 330 ohm resistor in series with a light emitting diode (LED). We will measure the current through the resistor and LED with an ammeter and we will measure the voltage across the resistor and LED with 2 voltmeters. Let us

observe:

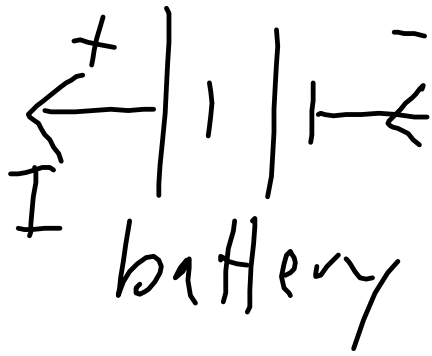

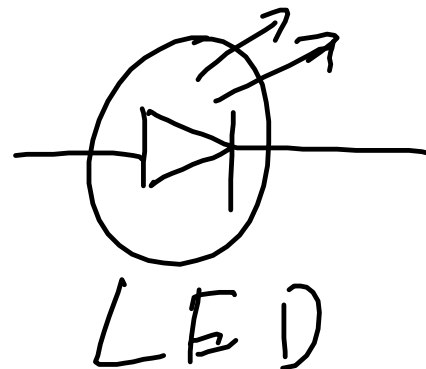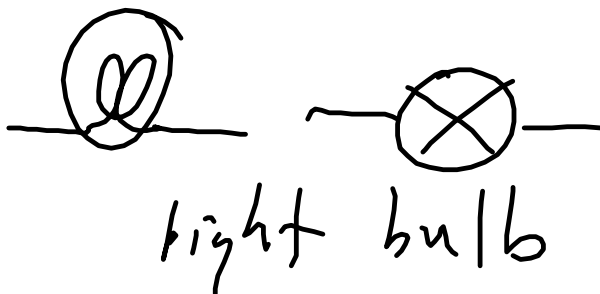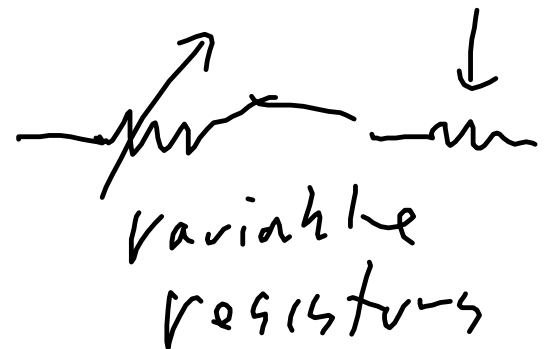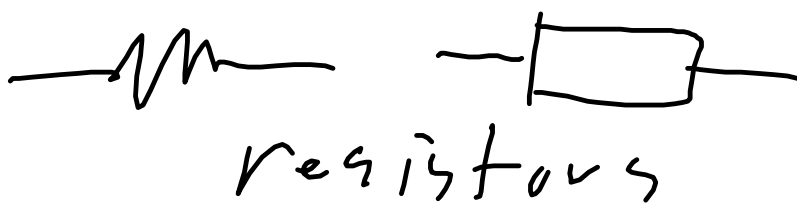I is conventional current
in amperes, A.
- electron flow is
opposite I .




Ammeter


* Series



Voltmeter


* Parallel

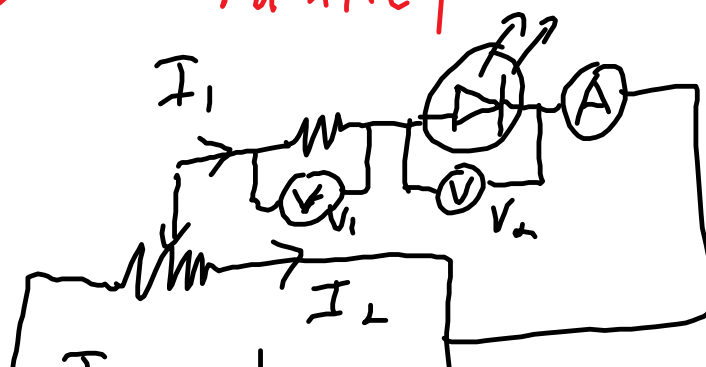

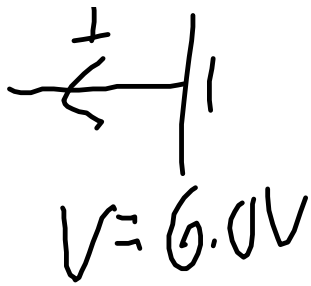

Voltage across resistor V_1 (V)	Voltage across diode V_2 (V)	Current through R + Diode I_1 (mA)
0.0	0.0	0.0
0.0	0.5	0.0
0.7	2.0	2.2
1.2	2.0	3.9
2.1	2.1	6.6
3.0	2.1	9.2
3.8	2.1	11.4

Resistor

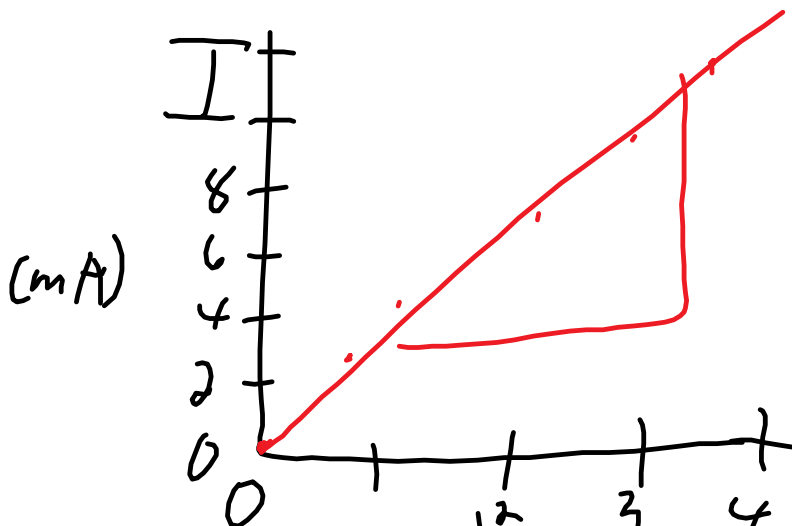



Resistance, R is ratio of Voltage across a circuit element to the current through the element.

$$R = V/I$$

Ohm's Law $V = IR$ is just a definition of resistance.

Units: Ohms, Ω

$$1 \Omega = V/A$$

Resistor - a circuit element that dissipates electrical energy as heat. Made to have a constant resistance over a range of V and I . "Ohmic" resistance is constant.

Diode - circuit element made of semiconductors that has many functions - LEDs give off light with limited heat given off.





Resistance is not constant.

Power, P

Is the rate of doing work or change energy.

$P = \text{energy/time}$ $V = \text{energy/charge}$ $I = \text{charge/time}$

$VI = \text{energy}/\cancel{q} \times \cancel{q}/t = \text{energy/time}$

$P = VI = V^2/R = I^2R$ from $V = IR$

From our data

Voltage across the resistor is 3.0V when the current is 9.2 mA and the voltage across the diode is 2.1V. Determine

- The resistance of each circuit element
- The power output of each device
- Repeat for $V_1 = 1.2V$ $I_1 = 3.9mA$ $V_2 = 2.0V$

a) $R = V/I$ $3.0V/9.2mA = 0.3261k\Omega =$ resistor: 330Ω

$R = 2.1/9.2 = 0.2283$ diode: 230Ω

b) $P = VI$ $3 \times 9.2 = 27.6$ 28mW resistor

$2.1 \times 9.2 = 19.32$ 19mW

c) $1.2/3.9 = 0.3077$ resistor 310Ω

$R = 1.2/9.2 = 0.1304$ diode: 130Ω

d) $P = VI$ $1.2 \times 3.9 = 4.68$ 4.7mW resistor

$2.0 \times 3.9 = 7.8$ 7.8mW diode

